



DCS Lab 4

Sequence


Finite state machine

郭晏誠


Mealy and Moore Machine

- Mealy machine
 - The outputs depend on the current state and inputs
- Moore machine
 - The outputs depend on the current state only



Mealy machine

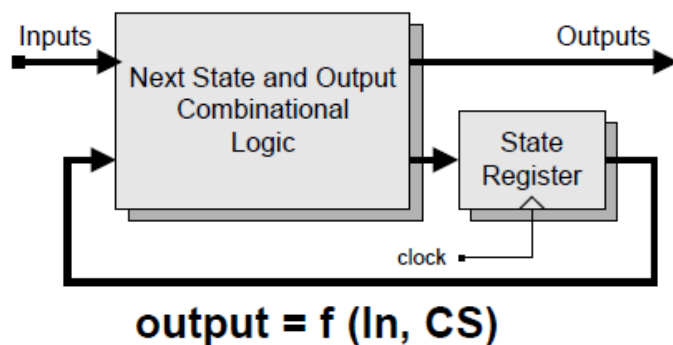

Moore machine

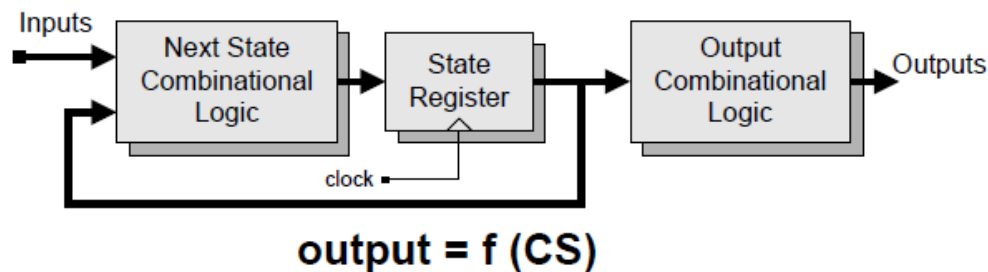

FSM coding style (example1)

  

```


input clk,rst_n,in_data;
output logic out;
logic [1:0] cur_state,next_state;
logic out_comb;
parameter S_0 = 2'd0;
parameter S_1 = 2'd1;
parameter S_2 = 2'd2;
parameter S_3 = 2'd3;

always_ff @(posedge clk or negedge rst_n) begin
    if(!rst_n) begin
        cur_state <= S_0;
    end else begin
        cur_state <= next_state;
    end
end

always_comb begin
    case(cur_state)
        S_0: next_state = ( in_data == 0 ) ? S_2 : S_1;
        S_1: next_state = ( in_data == 0 ) ? S_3 : S_1;
        S_2: next_state = ( in_data == 0 ) ? S_2 : S_3;
        S_3: next_state = ( in_data == 0 ) ? S_3 : S_3;
        default:next_state = cur_state;
    endcase
end

assign out_comb = ( next_state == S_3 ) ? 1 : 0;
always_ff @(posedge clk or negedge rst_n) begin
    if(!rst_n) begin
        out <= 0;
    end else begin
        out <= out_comb;
    end
end
end
  
```

FSM coding style (example2)

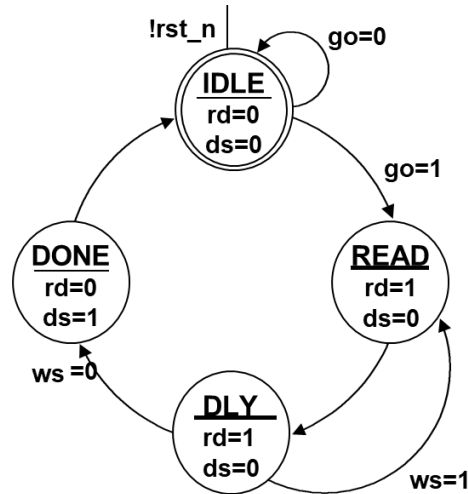

```

module fsm_cc1_2
(output logic rd, ds,
input go, ws, clk, rst_n);
//state parameter declaration
Parameter IDLE = 2'b00,
           READ = 2'b01,
           DLY  = 2'b11,
           DONE = 2'b10;

logic [1:0] curr_state, next_state;

always_ff@(posedge clk or negedge rst_n) begin
    if (!rst_n) curr_state <= IDLE;
    else curr_state <= next_state;
end
  
```


```

//next state and output logic
always_comb begin
    next = 'bx;
    rd = 1'b0;
    ds = 1'b0;
    case (curr_state)
    IDLE: begin
        if (go) next_state = READ;
        else next_state = IDLE;
    end
    READ: begin
        rd = 1'b1;
        next_state = DLY;
    end
    DLY : begin
        rd = 1'b1;
        if (!ws) next_state = DONE;
        else next_state = READ;
    end
    DONE: begin
        ds = 1'b1;
        next_state = IDLE;
    end
    endcase
end
endmodule
  
```


偵測Sequence 的設計

- Input 一個任意長度Sequence
- 設計FSM偵測任意長度Sequence
是否至少有3個bit是0和1個bit是1

參考FSM

 

in_state_reset

 

Seq.sv


Input Signal	Bit Width	Definition
clk	1	Clock
rst_n	1	Asynchronous active-low reset
in_data	1	FSM的input
in_state_reset	1	FSM的reset訊號 當in_state_reset == 1 , out_cur_state= $S_0(0)$

Output Signal	Bit Width	Definition
out_cur_state	3	FSM current state (每個cycle進行檢查) If (!rst_n) out_cur_state = $S_0(0)$ 當in_state_reset == 1 , out_cur_state= $S_0(0)$
out	1	FSM output (每個cycle進行檢查) If (!rst_n) out = 0 根據p6 FSM進行output

FSM example

Cycle	1	2	3	4	5	6	7	8	9	10	11
in_state_reset	1										
In_data	0										
out_cur_state		0									
out		0									


in_state_reset

 

FSM example

Cycle	1	2	3	4	5	6	7	8	9	10	11
in_state_reset	1	0									
In_data	0	0									
out_cur_state		0	2								
out		0	0								


in_state_reset

 

FSM example

Cycle	1	2	3	4	5	6	7	8	9	10	11
in_state_reset	1	0	0								
In_data	0	0	1								
out_cur_state		0	2	4							
out		0	0	0							


in_state_reset

 

FSM example

Cycle	1	2	3	4	5	6	7	8	9	10	11
in_state_reset	1	0	0	0							
In_data	0	0	1	1							
out_cur_state		0	2	4	4						
out		0	0	0	0						


in_state_reset

 

FSM example

Cycle	1	2	3	4	5	6	7	8	9	10	11
in_state_reset	1	0	0	0	0						
In_data	0	0	1	1	0						
out_cur_state		0	2	4	4	5					
out		0	0	0	0	0					


in_state_reset

 

FSM example

Cycle	1	2	3	4	5	6	7	8	9	10	11
in_state_reset	1	0	0	0	0	0					
In_data	0	0	1	1	0	0					
out_cur_state		0	2	4	4	5	7				
out		0	0	0	0	0	1				


in_state_reset

 

FSM example

Cycle	1	2	3	4	5	6	7	8	9	10	11
in_state_reset	1	0	0	0	0	0	0				
In_data	0	0	1	1	0	0	1				
out_cur_state		0	2	4	4	5	7	7			
out		0	0	0	0	0	1	1			


in_state_reset

 

FSM example

Cycle	1	2	3	4	5	6	7	8	9	10	11
in_state_reset	1	0	0	0	0	0	0	0			
In_data	0	0	1	1	0	0	1	0			
out_cur_state		0	2	4	4	5	7	7	7		
out		0	0	0	0	0	1	1	1		


in_state_reset

 

FSM example

Cycle	1	2	3	4	5	6	7	8	9	10	11
in_state_reset	1	0	0	0	0	0	0	0	0		
In_data	0	0	1	1	0	0	1	0	0		
out_cur_state		0	2	4	4	5	7	7	7	7	
out		0	0	0	0	0	1	1	1	1	


in_state_reset

 

FSM example

Cycle	1	2	3	4	5	6	7	8	9	10	11
in_state_reset	1	0	0	0	0	0	0	0	0	1	
In_data	0	0	1	1	0	0	1	0	0	0	
out_cur_state		0	2	4	4	5	7	7	7	7	0
out		0	0	0	0	0	1	1	1	1	0

in_state_reset

 


Spec

- 請使用FSM完成此次LAB，可參考pg 6。
- 所有output必須非同步負準位reset。
- 01_RTL 需要PASS。
- 02_SYN不能有error跟latches。
- 02_SYN時間timing slack必須為MET。
- 03_GATE 需要PASS

Waveform rst_n

- Waveform

 


negative trigger asynchronous reset

Waveform 1st in_state_reset

- Waveform


FSM reset, out_cur_state = 0, out = 0

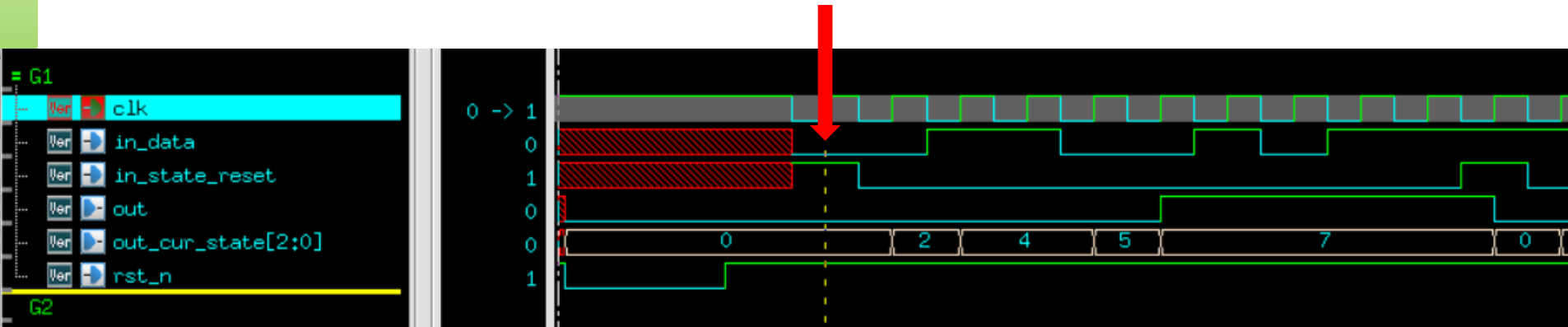

Waveform in_data

- Waveform


FSM, 參考p7~p17

 

Waveform 2nd in_state_reset

- Waveform

FSM reset, out_cur_state = 0, out = 0

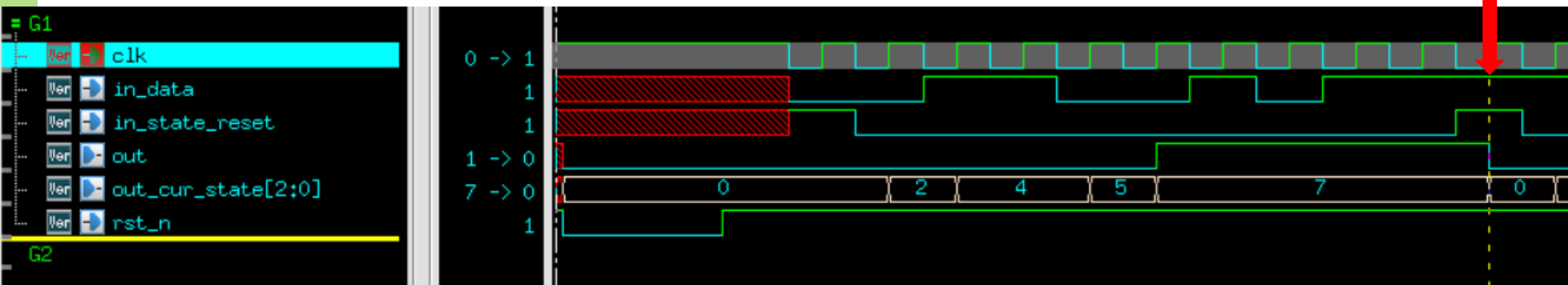

Command

- 不要更改FSM state parameter

```
12 //-----  
13 //   INPUT AND OUTPUT DECLARATION  
14 //-----  
15 input clk,rst_n,in_data,in_state_reset;  
16 output logic [2:0] out_cur_state;  
17 output logic out;  
18  
19  
20 //-----  
21 //   FSM state  
22 //-----  
23 parameter S_0 = 3'd0;  
24 parameter S_1 = 3'd1;  
25 parameter S_2 = 3'd2;  
26 parameter S_3 = 3'd3;  
27 parameter S_4 = 3'd4;  
28 parameter S_5 = 3'd5;  
29 parameter S_6 = 3'd6;  
30 parameter S_7 = 3'd7;  
31  
32 //-----  
33 //   Your design  
34 //-----  
35  
36  
37  
38  
39
```

Command

- `tar -xvf ~dcsta01/Lab04.tar`
- `cd Lab04/01_RTL/`
- Need 02_SYN
 - No Latch
 - No error
 - No timing violation (MET)
- Need 03_GATE
- Separate combinational and sequential blocks

Demo1: 3/24(四), 16:25:00

Demo2: 3/24(四), 23:59:59