




DCS Lab 5

AHB interconnect

Finite state machine

蔣洛亘


Flow Control: ready-valid flow

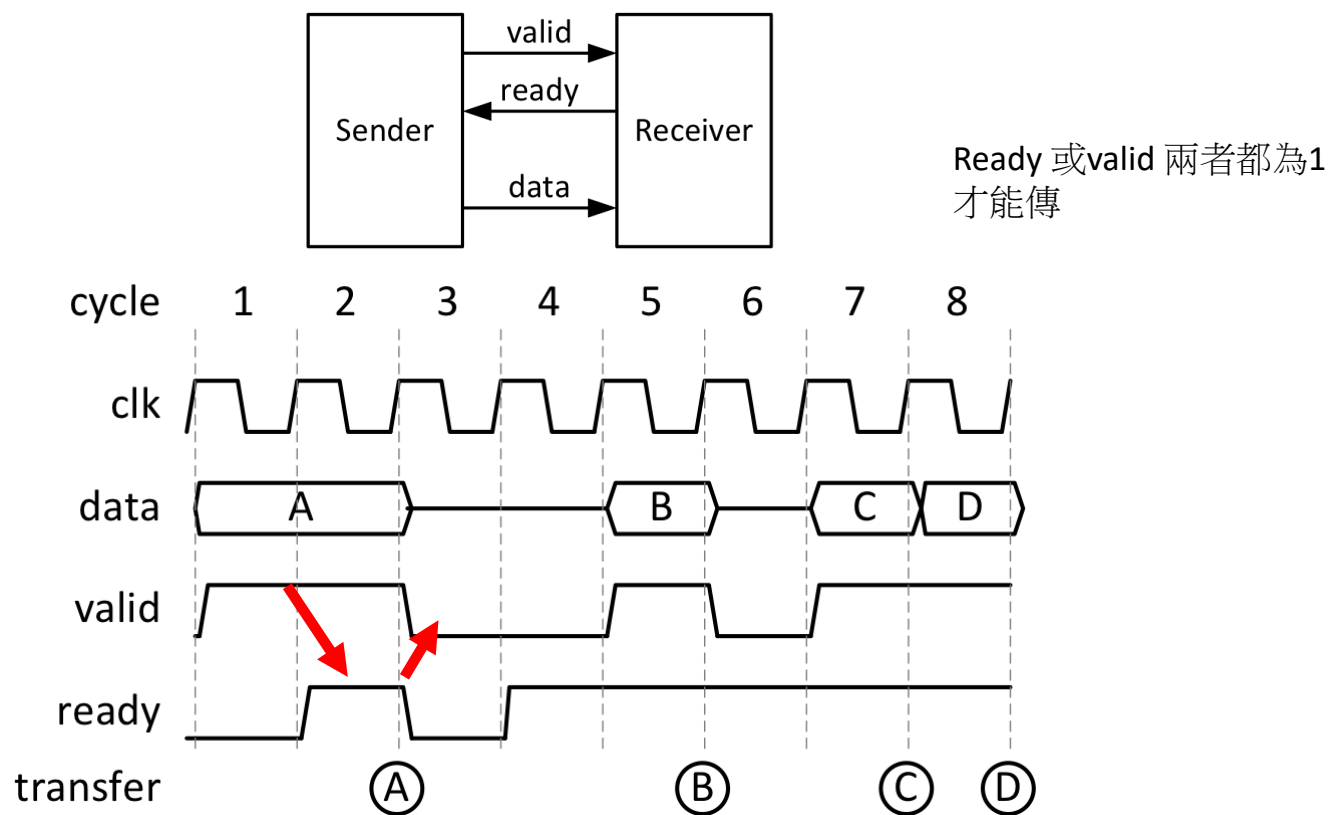


Handshake process

- Ready before valid / Valid before ready
- Valid with ready


handshake

 

handshake

 


handshake

 

If(valid && ready)

AHB Interconnect

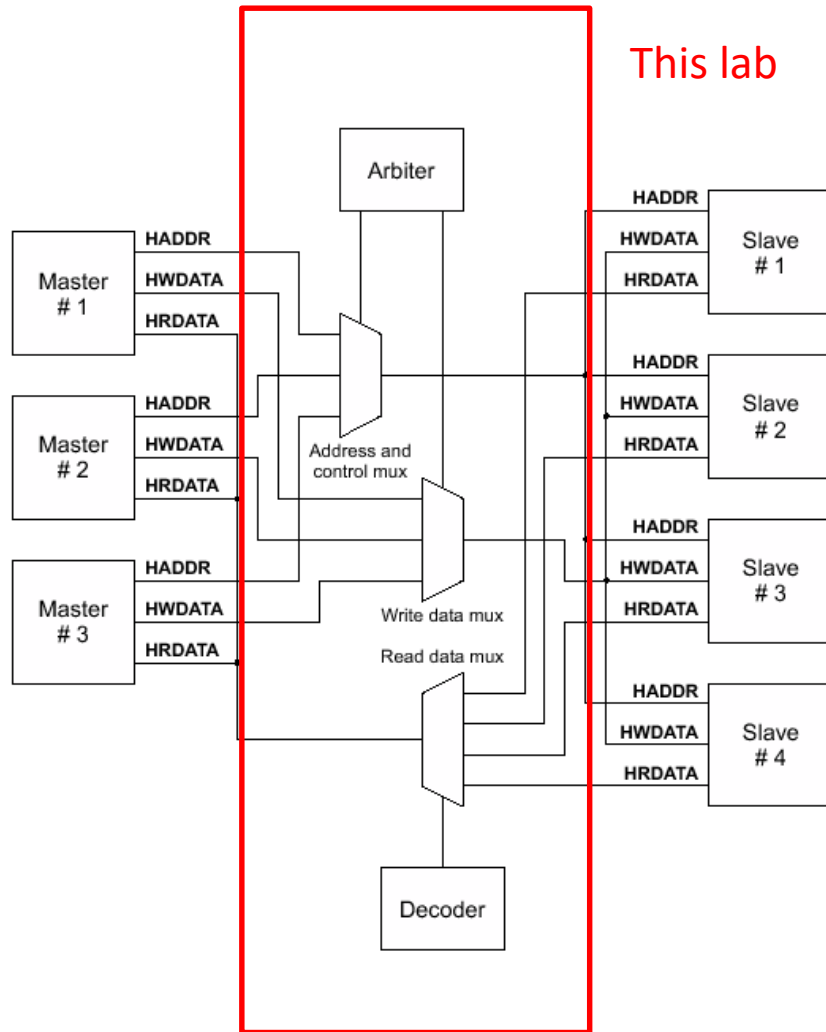


Basic components:

- Master
- Slave
- Arbiter
- Decoder
- Mux

Lab - block diagram

Pattern

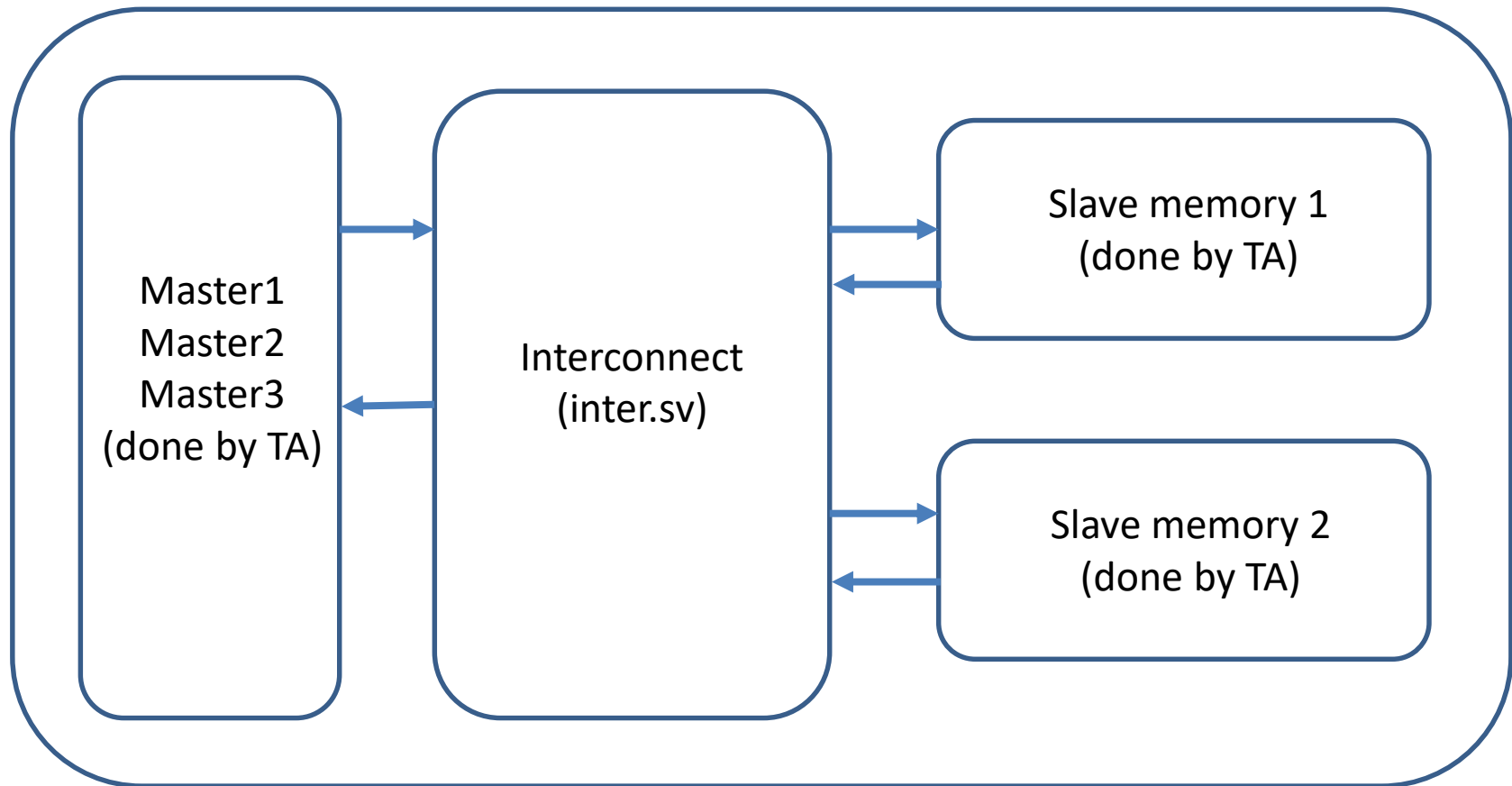

Lab

- Masters will send input data to interconnect
- You should decode input data for valid, address and value
- Based on **master priority(1->2->3)**, send data to slave memory
- Output handshake signal

Lab - decode

- [6:0]data_in_1 (from Master1)
- data_in_1[6]: 0->slave1 1->slave2
- data_in_1[5:3]: address
- data_in_1[2:0]: value
- Ex: 7'b0101001 for slave1, addr=5, value=1
- Ex: 7'b1011110 for slave2, addr=3, value=6


inter.sv

Input Signal	Bit Width	Definition
clk	1	Clock
rst_n	1	Asynchronous active-low reset
in_valid_1	1	in_valid from master1
in_valid_2	1	in_valid from master2
in_valid_3	1	in_valid from master3
data_in_1	7	Data from master1
data_in_2	7	Data from master2
data_in_3	7	Data from master3
ready_slave1	1	Ready signal from slave1
ready_slave2	1	Ready signal from slave2

inter.sv

Output Signal	Bit Width	Definition
valid_slave1	1	valid signal to slave1
valid_slave2	1	valid signal to slave2
addr_out	3	Address you want to write
value_out	3	Value you want to save
handshake_slave1	1	High for 1 cycle after handshake with slave1
handshake_slave2	1	High for 1 cycle after handshake with slave2


Lab – Arbiter FSM (ref.)

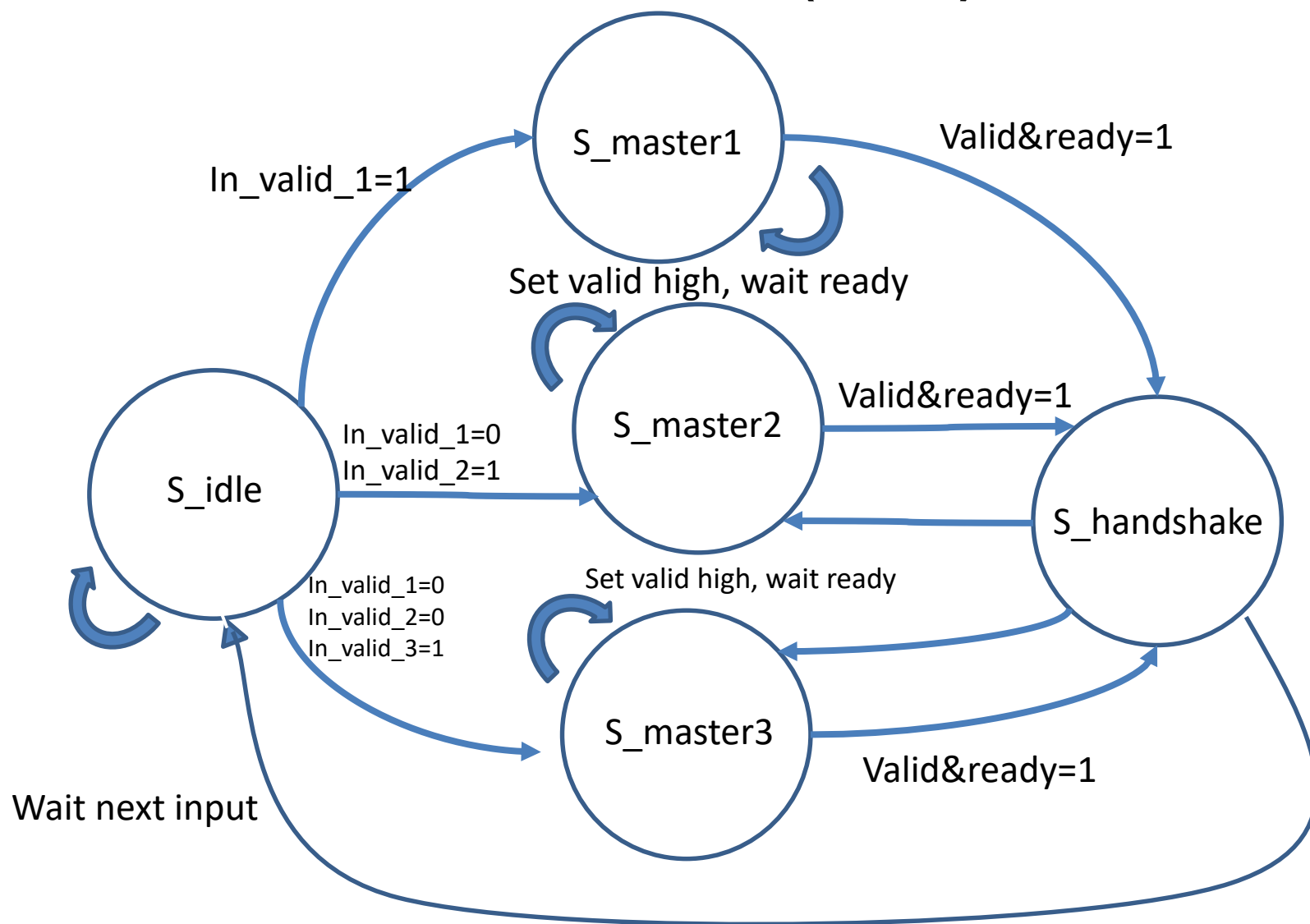

Spec


- 不可以超過30個cycles沒有完成handshake(從invalid或上一次handshake開始數)
- 拉起handshake signal(**only 1 cycle**)後,pattern會檢查全部slave memory的值，必須依照master priority
- 可參考助教提供的FSM。
- 所有output必須非同步負準位reset。
- 01_RTL 需要PASS。
- 02_SYN不能有error跟latches。
- 02_SYN時間timing slack必須為MET。
- 03_GATE 需要PASS

Waveform

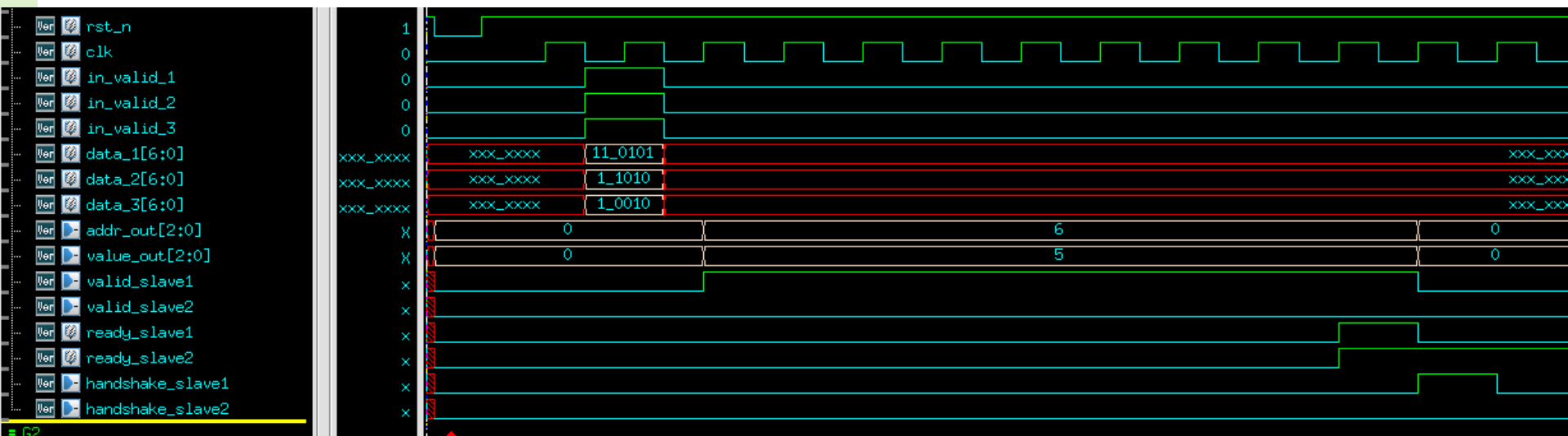


negative trigger asynchronous reset

Waveform

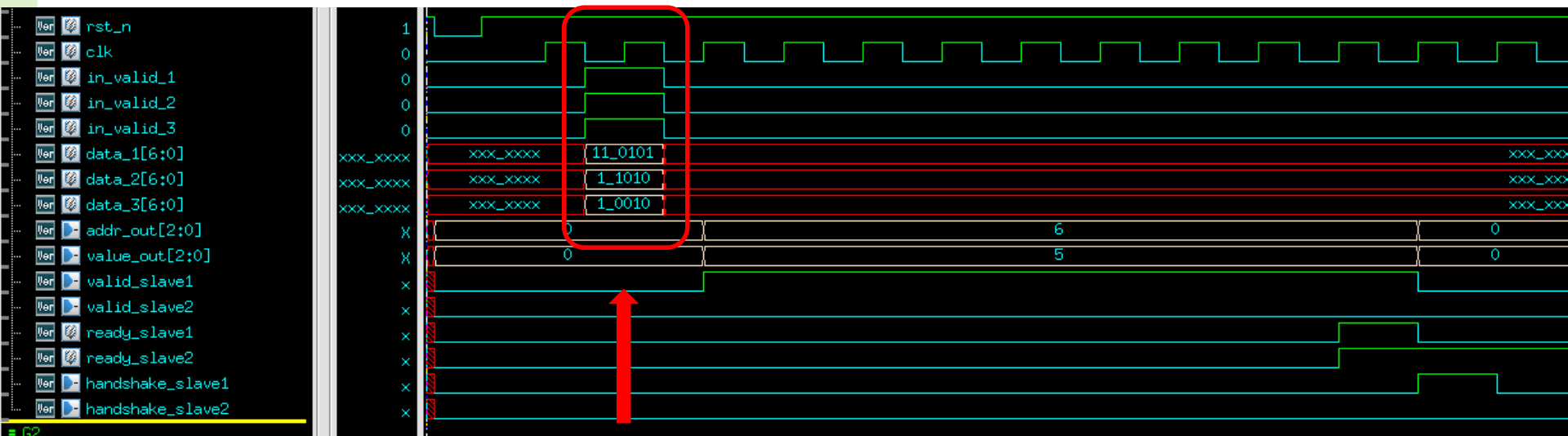

Input data


Waveform

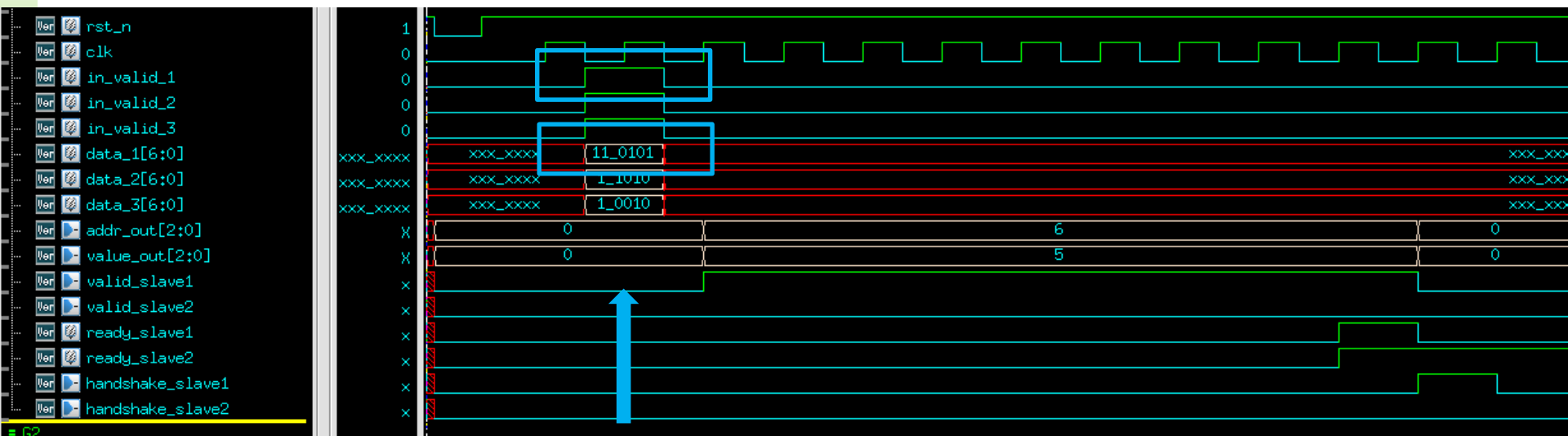

Master1 first


Decode: 0 110 101 => slave1 address:6 value:5

Waveform

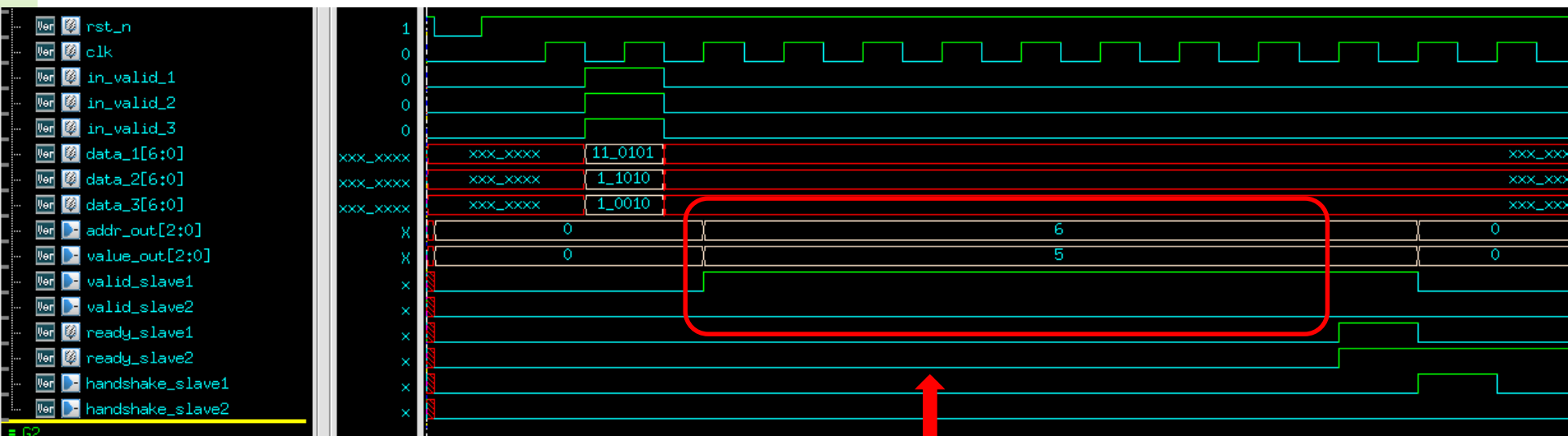


Set valid high, wait slave1 ready

Waveform

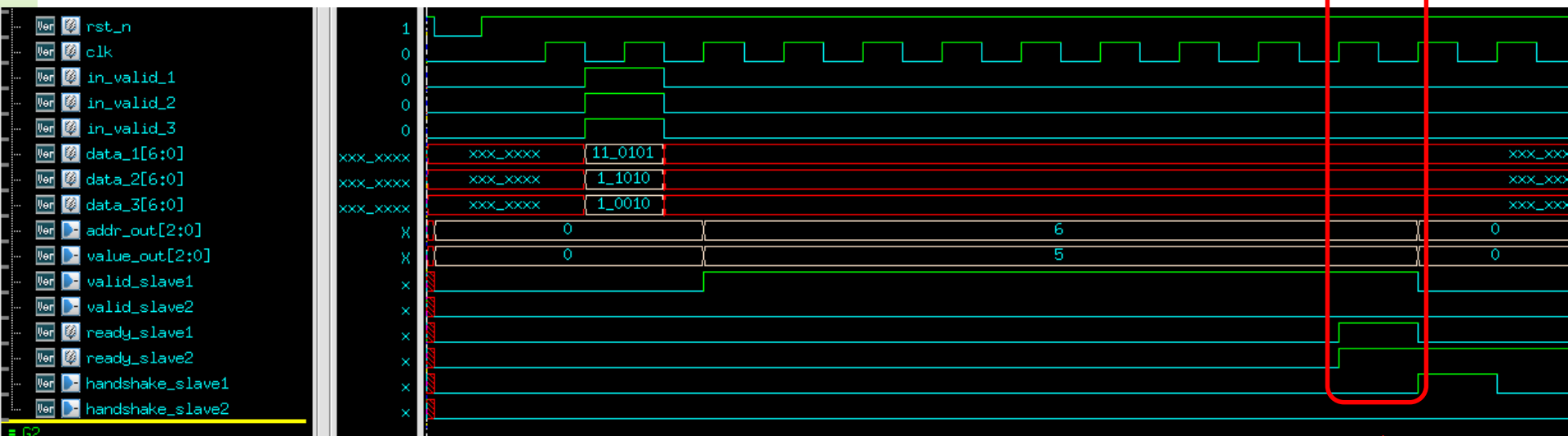

Handshake!


Waveform

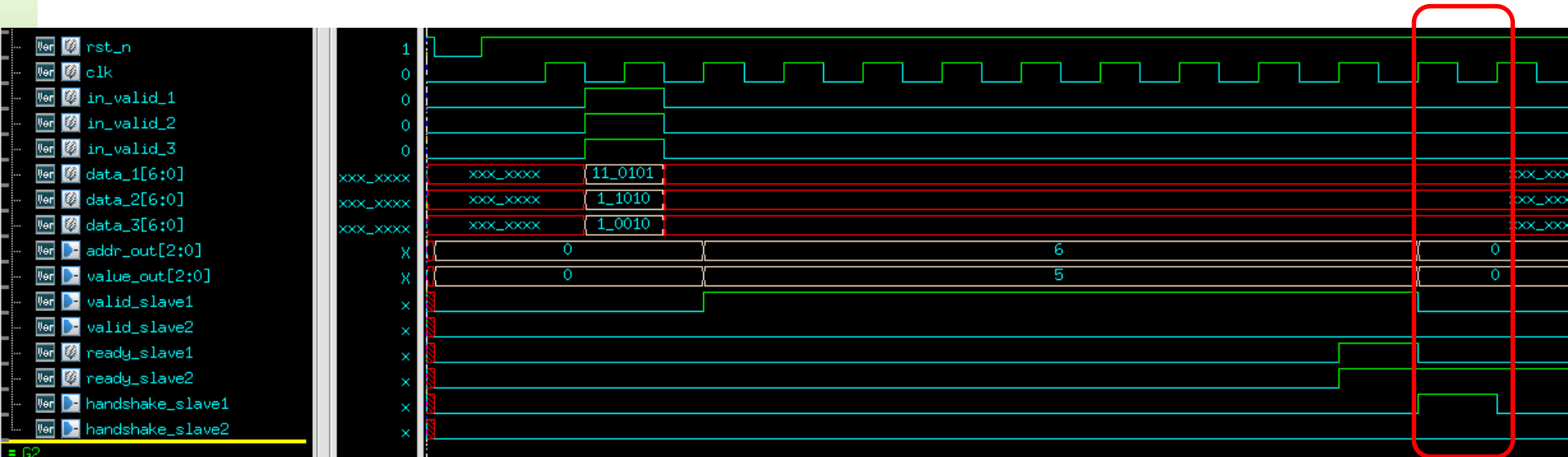


output handshake signal

Waveform

Continue for Master2

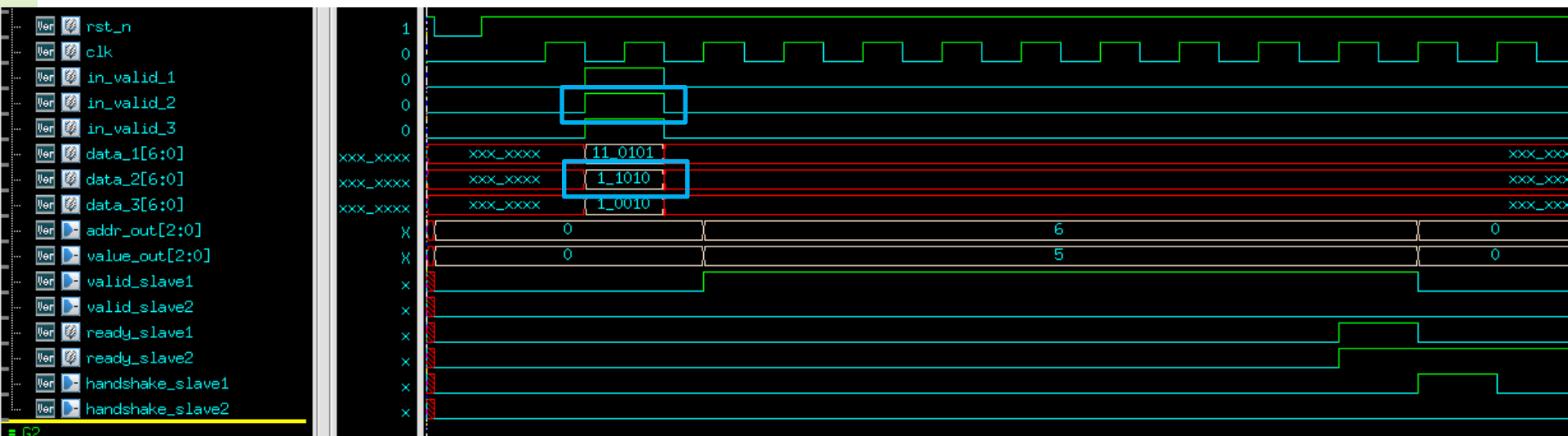

Waveform

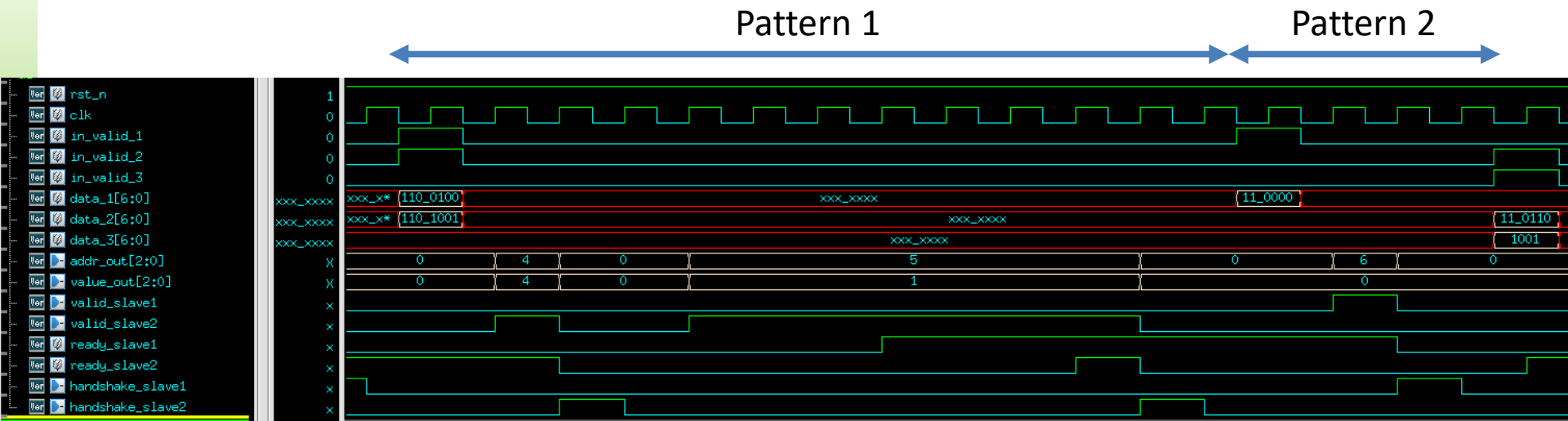

Command

- `tar -xvf ~dcsta01/Lab05.tar`
- `cd Lab05/01_RTL/`
- Need 02_SYN
 - No Latch
 - No error
 - No timing violation (MET)
- Need 03_GATE
- Separate combinational and sequential blocks

Demo1: 3/31(四), 16:25:00

Demo2: 3/31(四), 23:59:59